

Diode Application

Dr Mohammad Abdur Rashid




Readings

Electronic Devices and Circuit Theory – Boylestad, Nashelsky

Chapter 2: Diode Applications




Diode

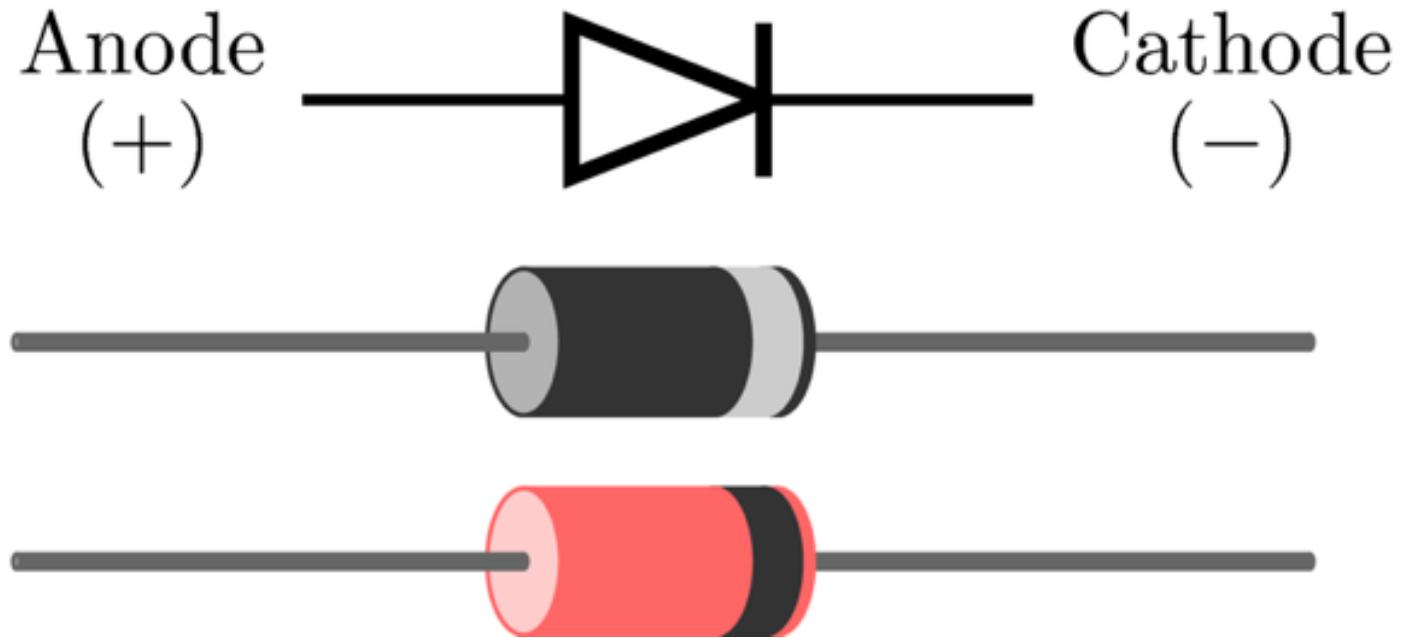

Current versus voltage characteristics

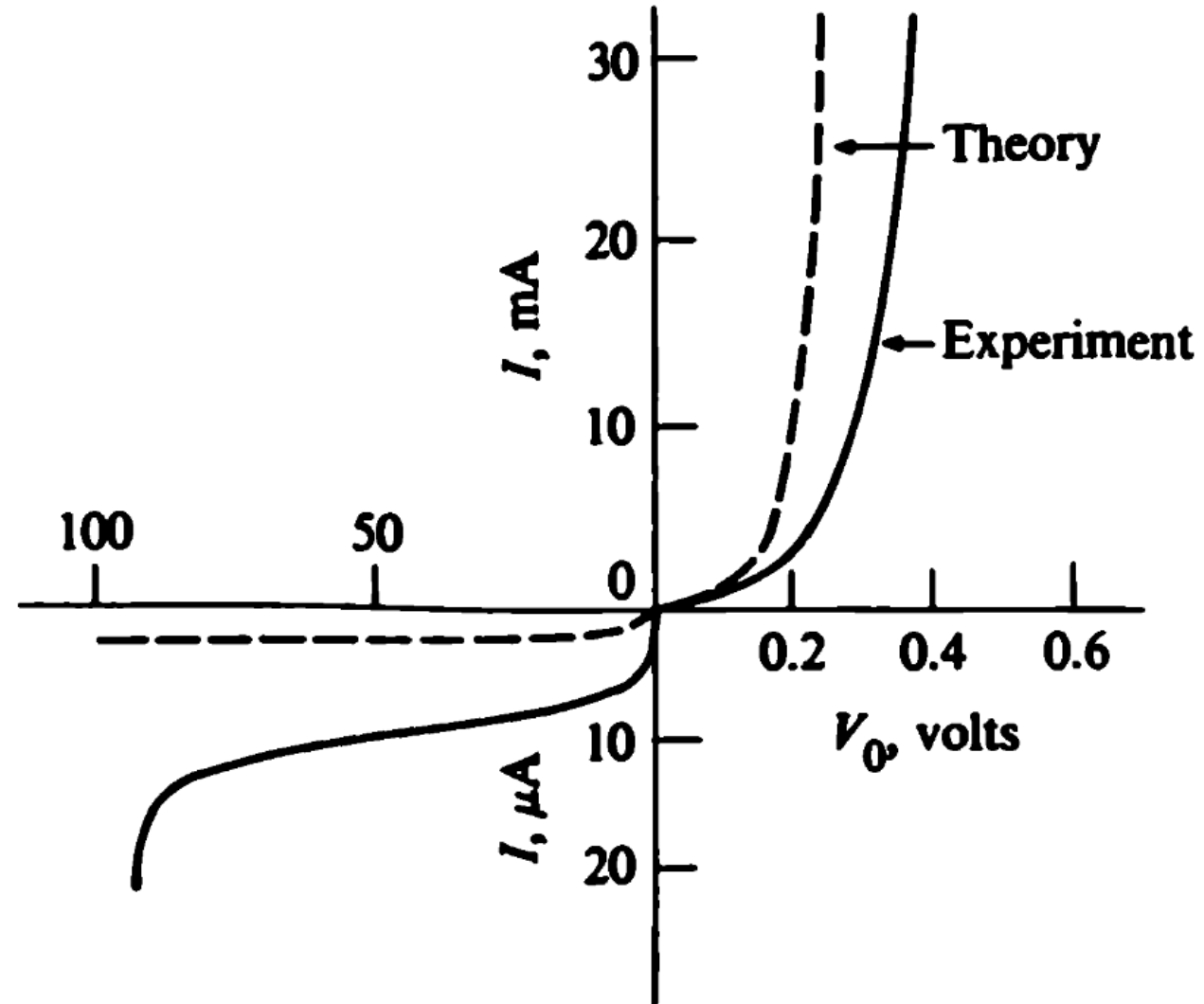Elementary Solid State
Physics – Ali Omar




LED residential and commercial lighting



Electronic Devices and Circuit Theory – Boylestad, Nashelsky





Diode symbol

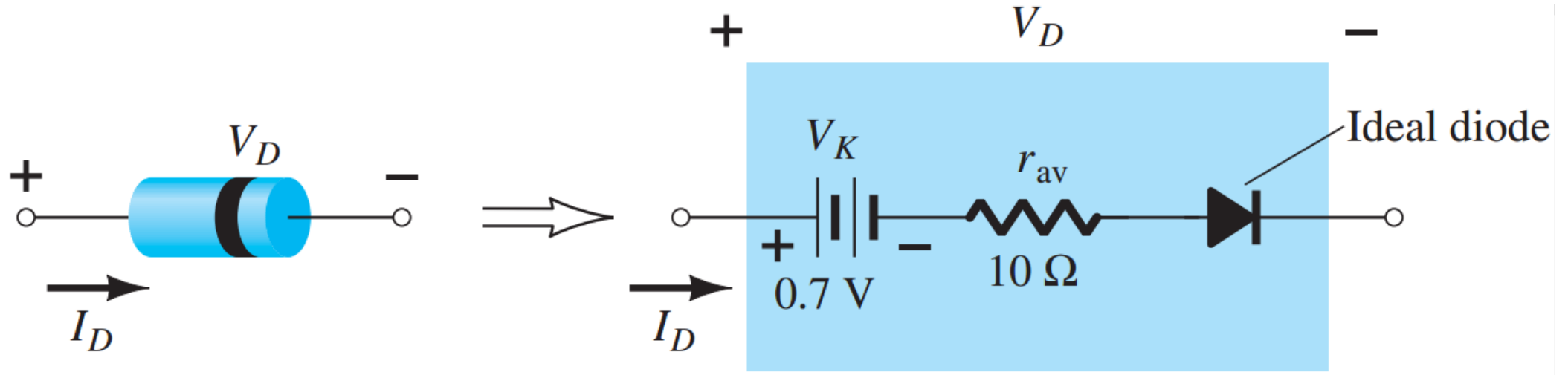

Electronic Devices and Circuit Theory – Boylestad, Nashelsky



Load-line analysis

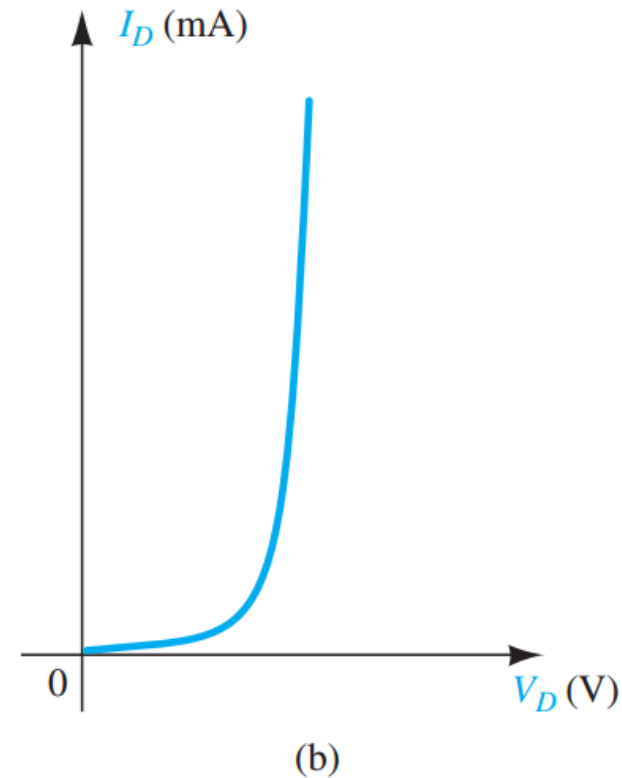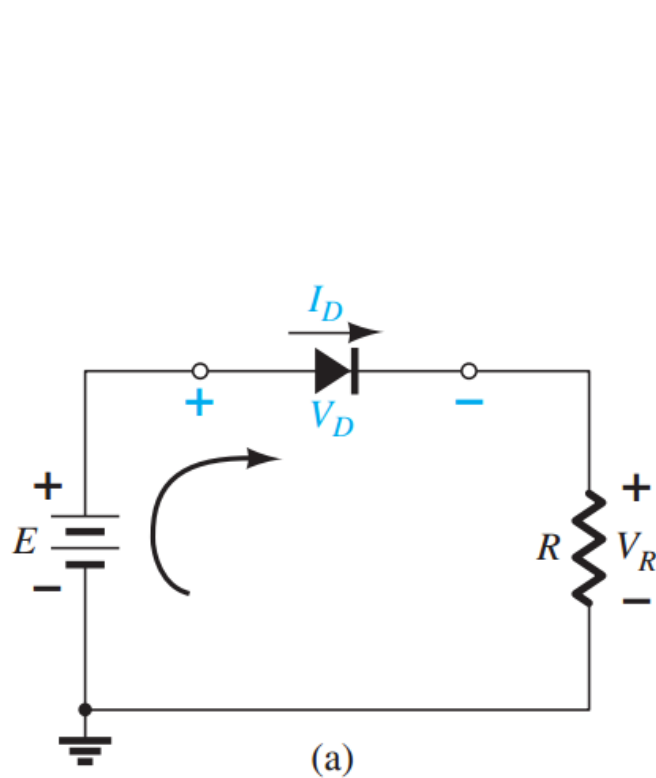

Electronic Devices and Circuit Theory – Boylestad, Nashelsky


Series diode configuration: (a) circuit; (b) characteristics.

Note

In general, a diode is in the “on” state if the current established by the applied sources is such that its direction matches that of the arrow in the diode symbol, and $V_D \geq 0.7$ V for silicon, $V_D \geq 0.3$ V for germanium, and $V_D \geq 1.2$ V for gallium arsenide.



Applying Kirchhoff's voltage law

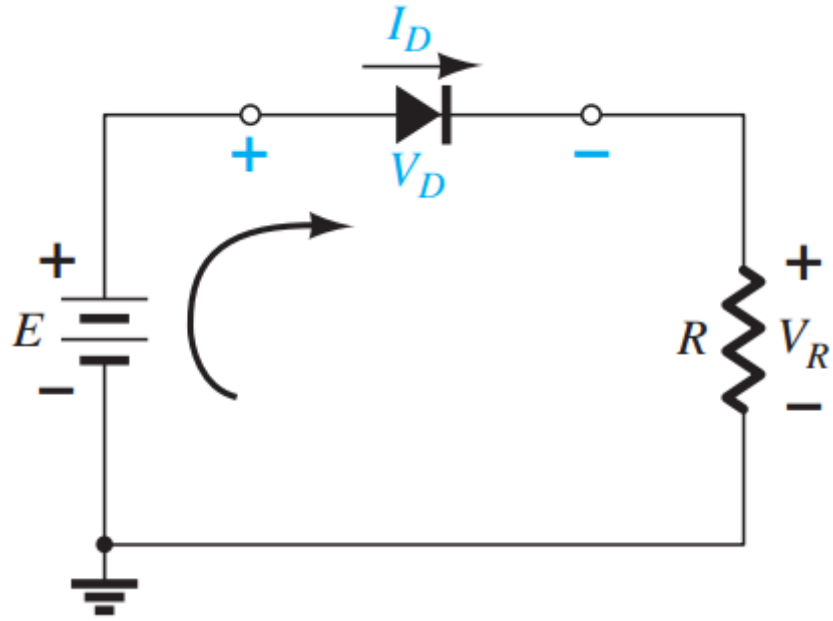


$$E = V_D + I_D R$$

$$I_D = \frac{E}{R} \Big|_{V_D=0 \text{ V}}$$

$$V_D = E \Big|_{I_D=0 \text{ A}}$$

Load line and point of operation

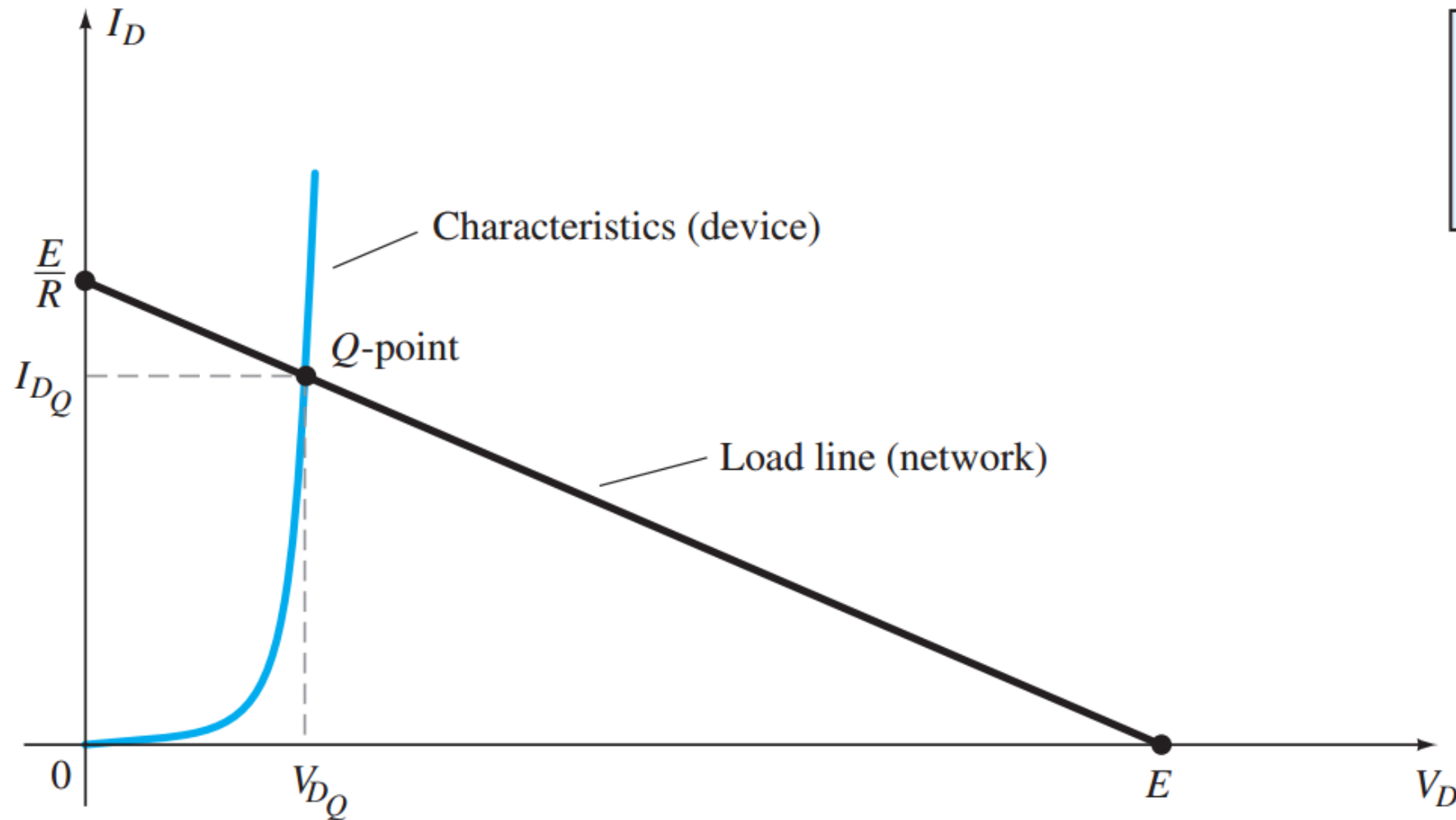


$$I_D = \frac{E}{R} \Big|_{V_D=0 \text{ V}}$$

$$V_D = E \Big|_{I_D=0 \text{ A}}$$





Q-point

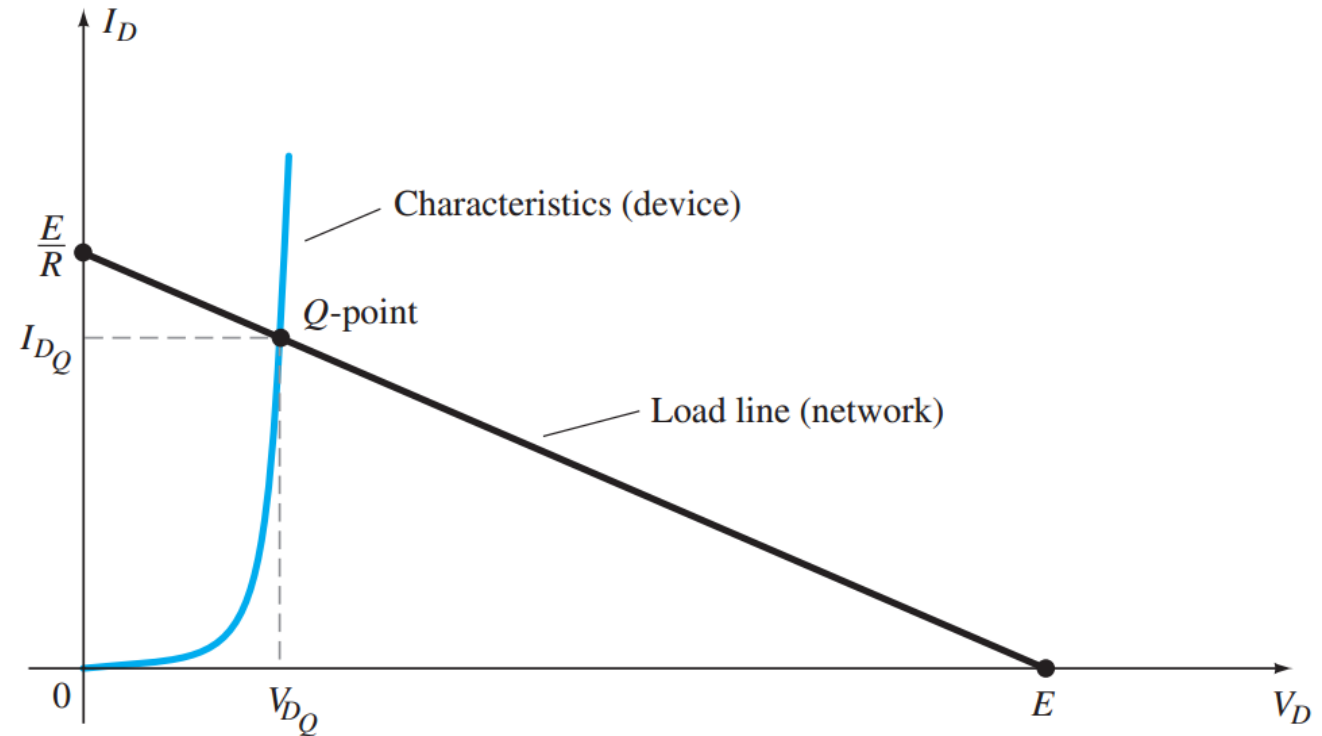The point of operation is usually called the quiescent point (abbreviated “Q-point”) to reflect its “still, unmoving” qualities as defined by a dc network.




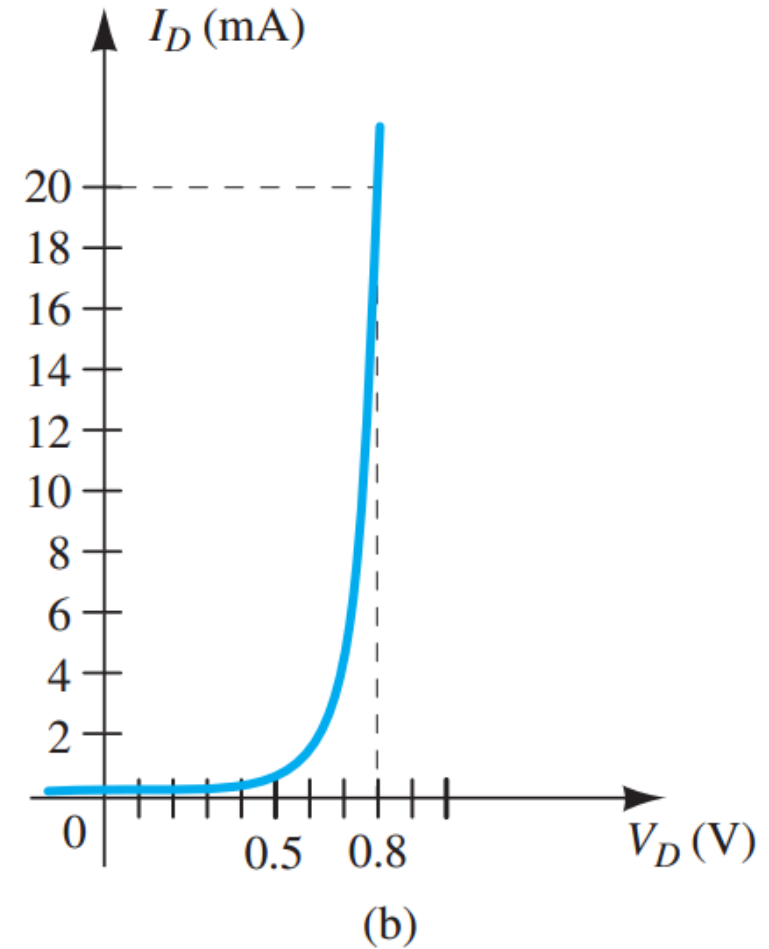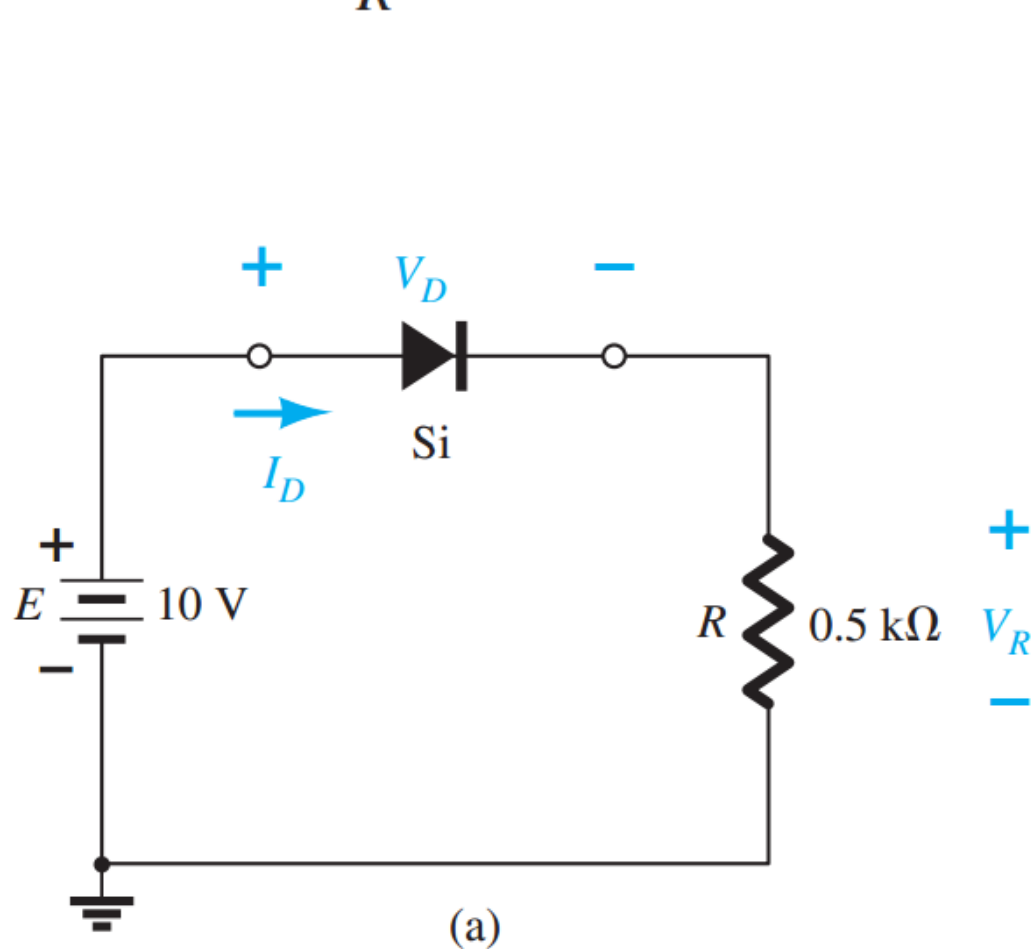Determine: a. V_{D_Q} and I_{D_Q} .
b. V_R .



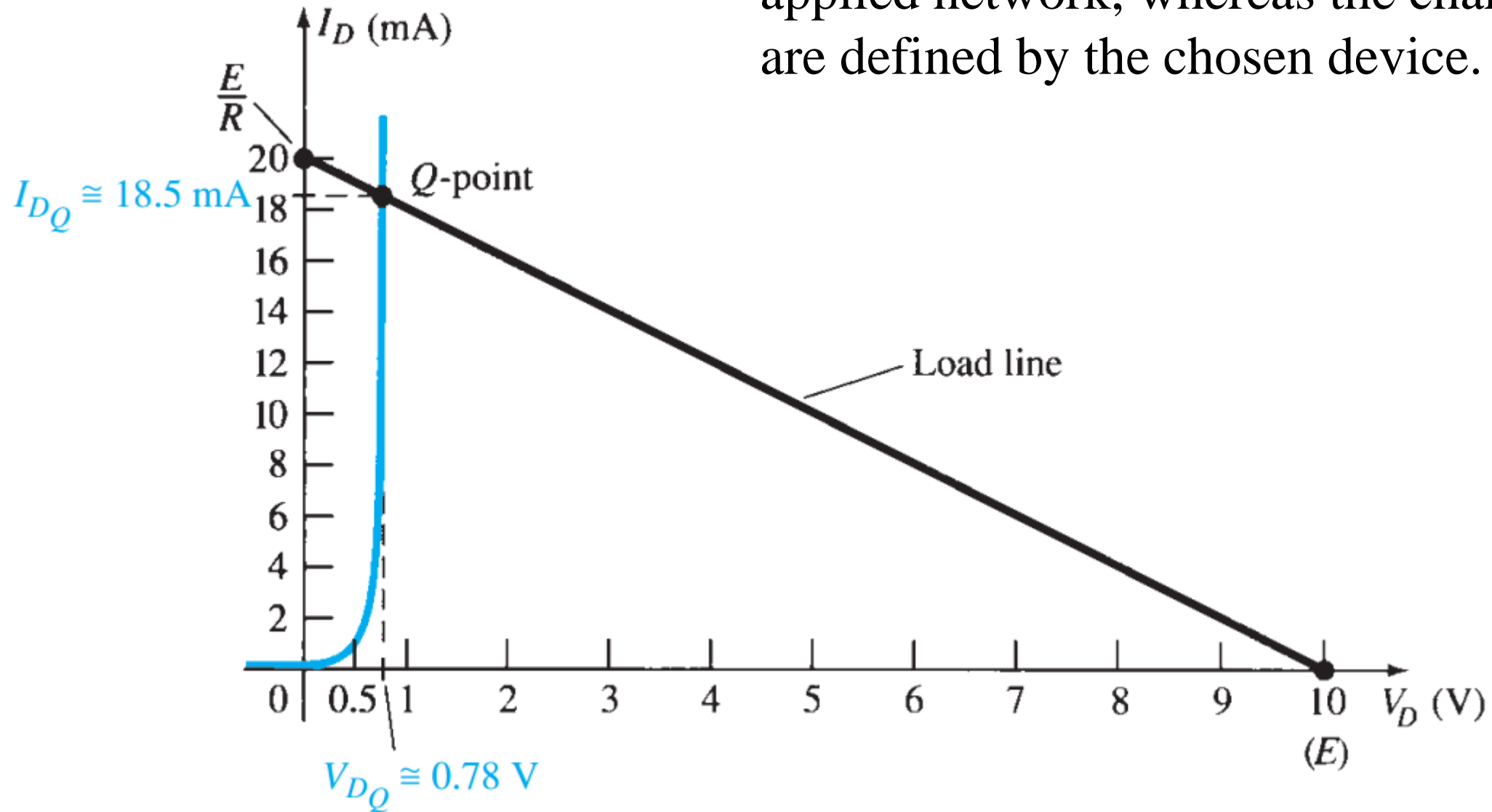
(a) Circuit; (b) characteristics.


The load line is determined solely by the applied network, whereas the characteristics are defined by the chosen device.



Using the Q -point values, the dc resistance
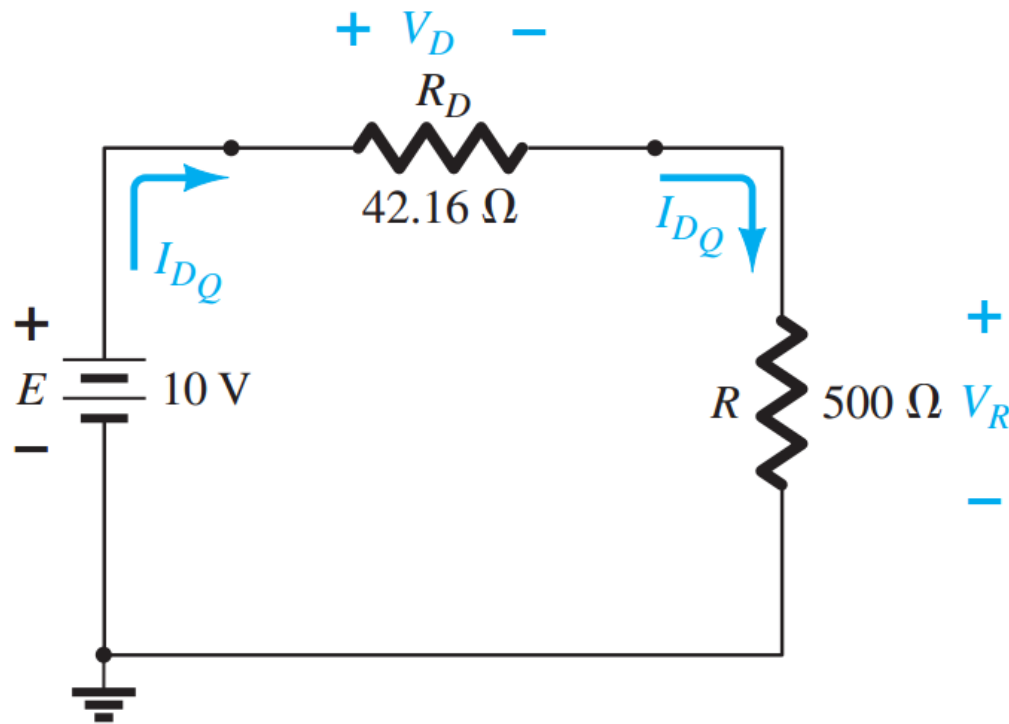
$$R_D = \frac{V_{DQ}}{I_{DQ}} = \frac{0.78 \text{ V}}{18.5 \text{ mA}} = 42.16 \Omega$$



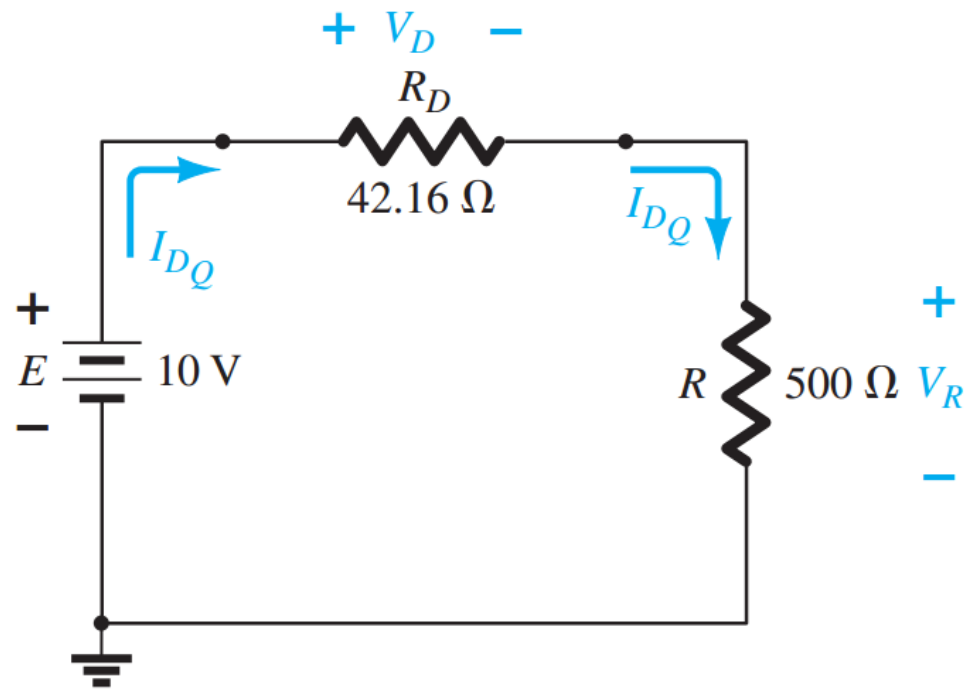


$$I_D = \frac{E}{R_D + R} = \frac{10\text{ V}}{42.16\ \Omega + 500\ \Omega} = \frac{10\text{ V}}{542.16\ \Omega} \cong \mathbf{18.5\text{ mA}}$$

$$V_R = \frac{RE}{R_D + R} = \frac{(500\ \Omega)(10\text{ V})}{42.16\ \Omega + 500\ \Omega} = \mathbf{9.22\text{ V}}$$




Half-wave rectifier

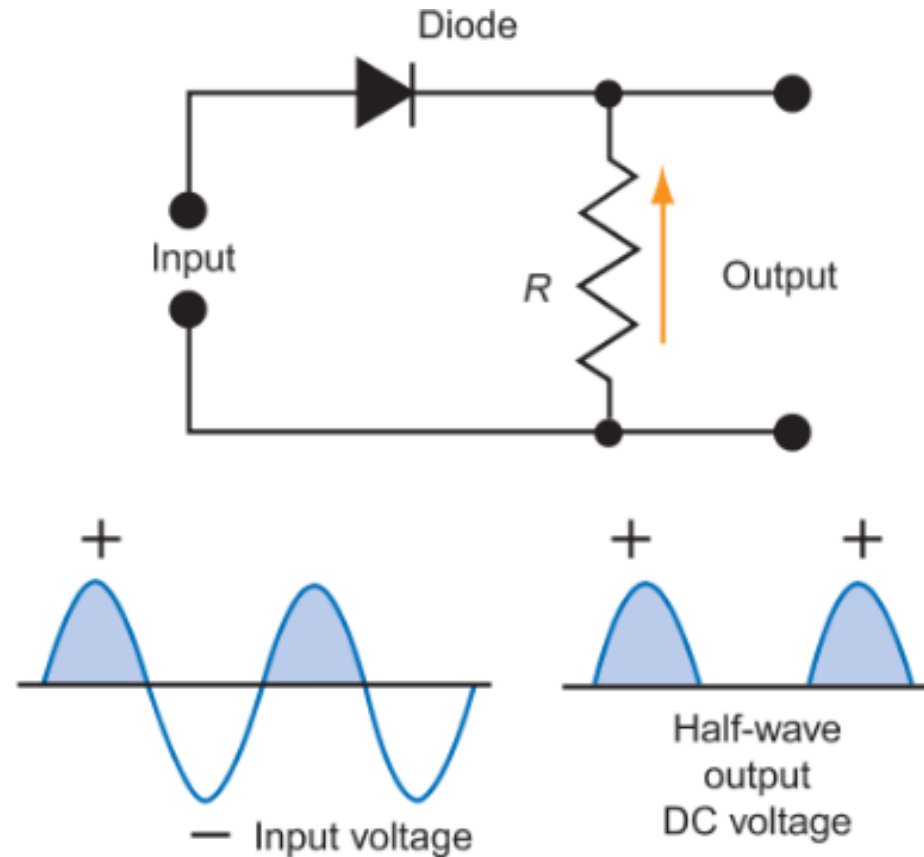

electricala2z.com




Half-wave rectifier

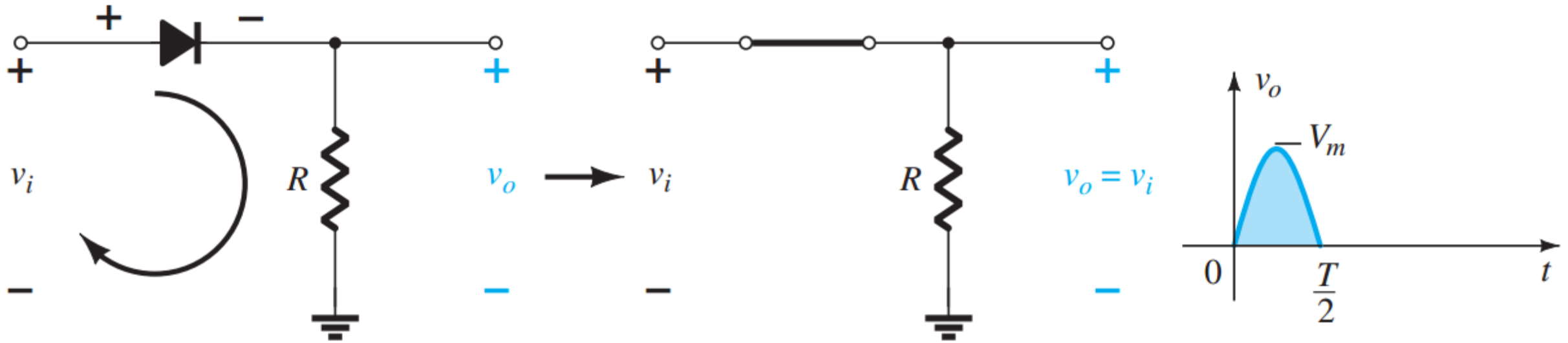

Electronic Devices and Circuit Theory – Boylestad, Nashelsky




Half-wave rectifier

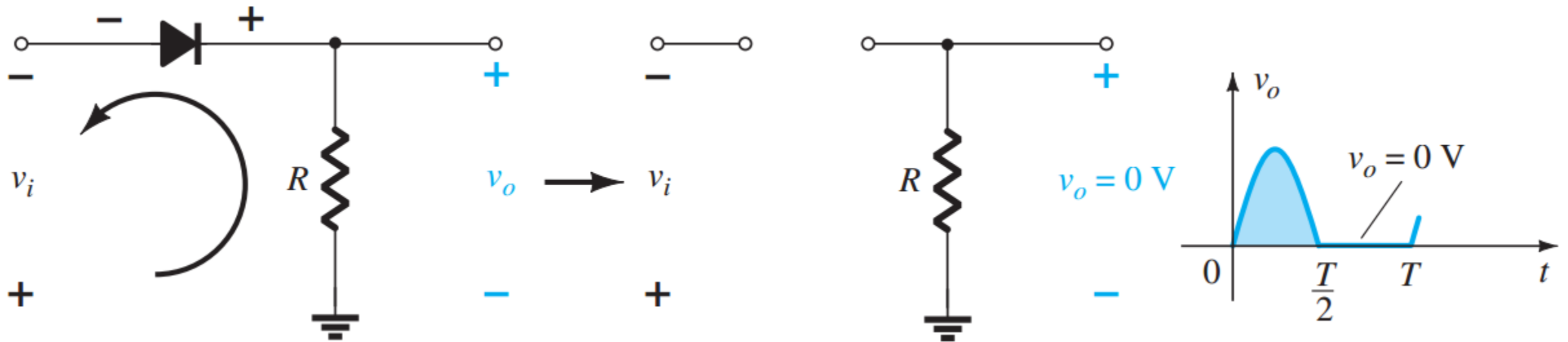

Electronic Devices and Circuit Theory – Boylestad, Nashelsky






Half-wave rectified signal

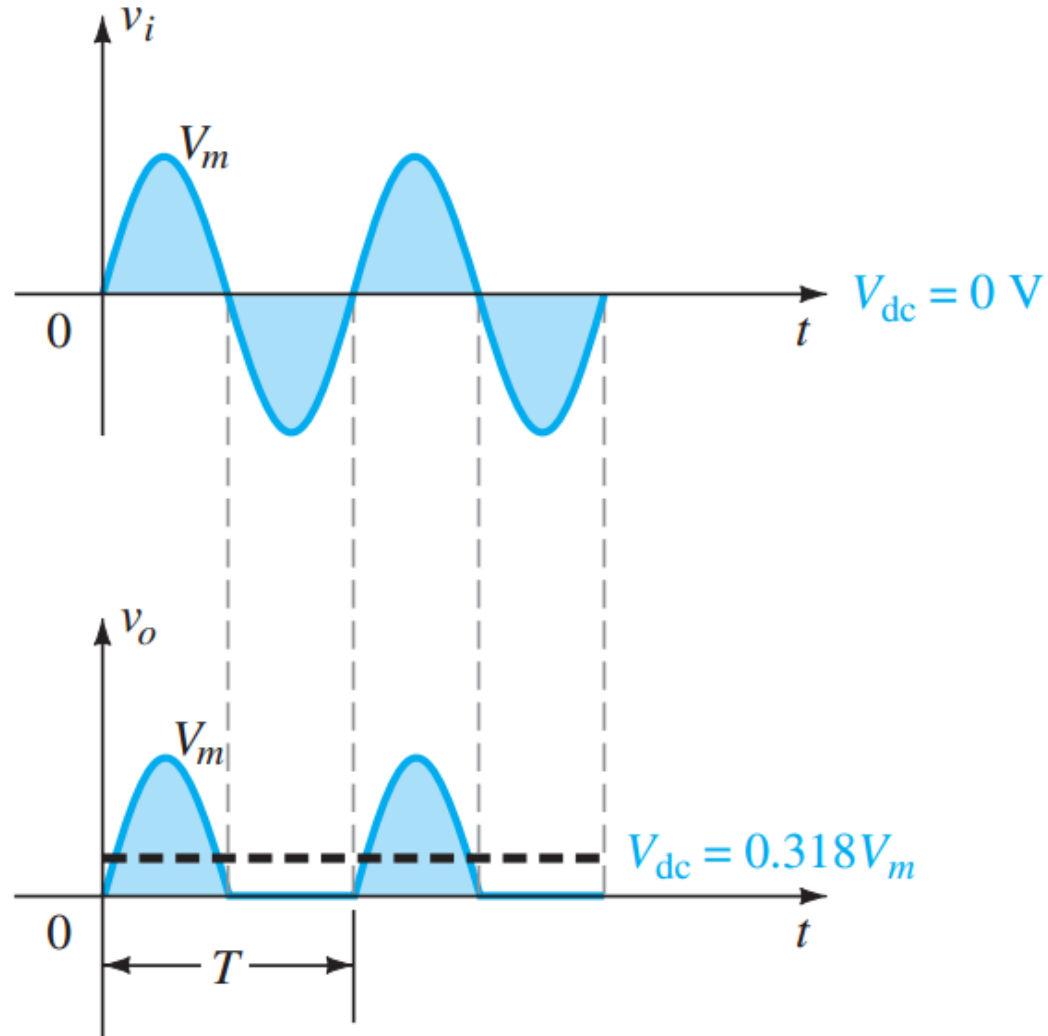

Electronic Devices and Circuit Theory – Boylestad, Nashelsky



Half-wave rectified signal

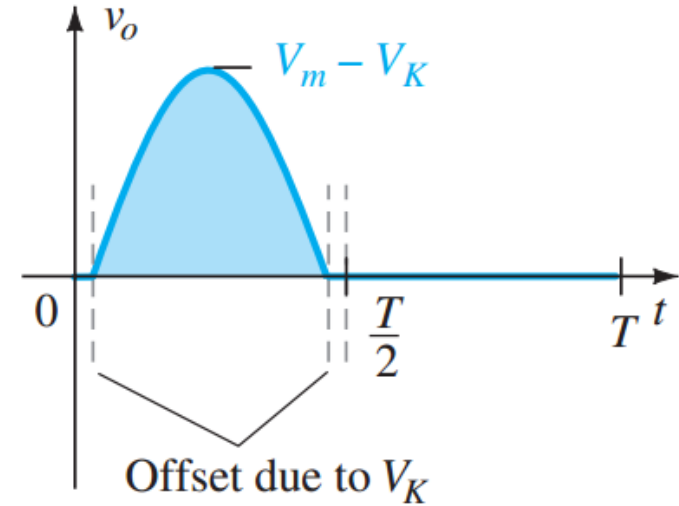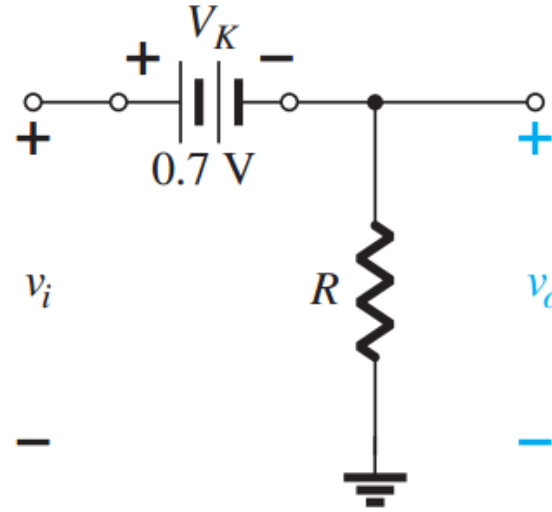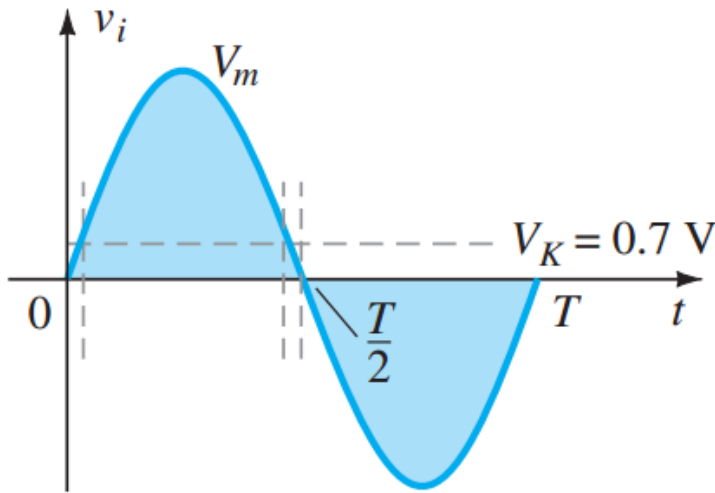


$$V_{dc} \cong 0.318(V_m - V_K)$$

Electronic Devices and Circuit Theory – Boylestad, Nashelsky



Alternating current (AC)

$$V(t) = V_m \sin(\omega t)$$

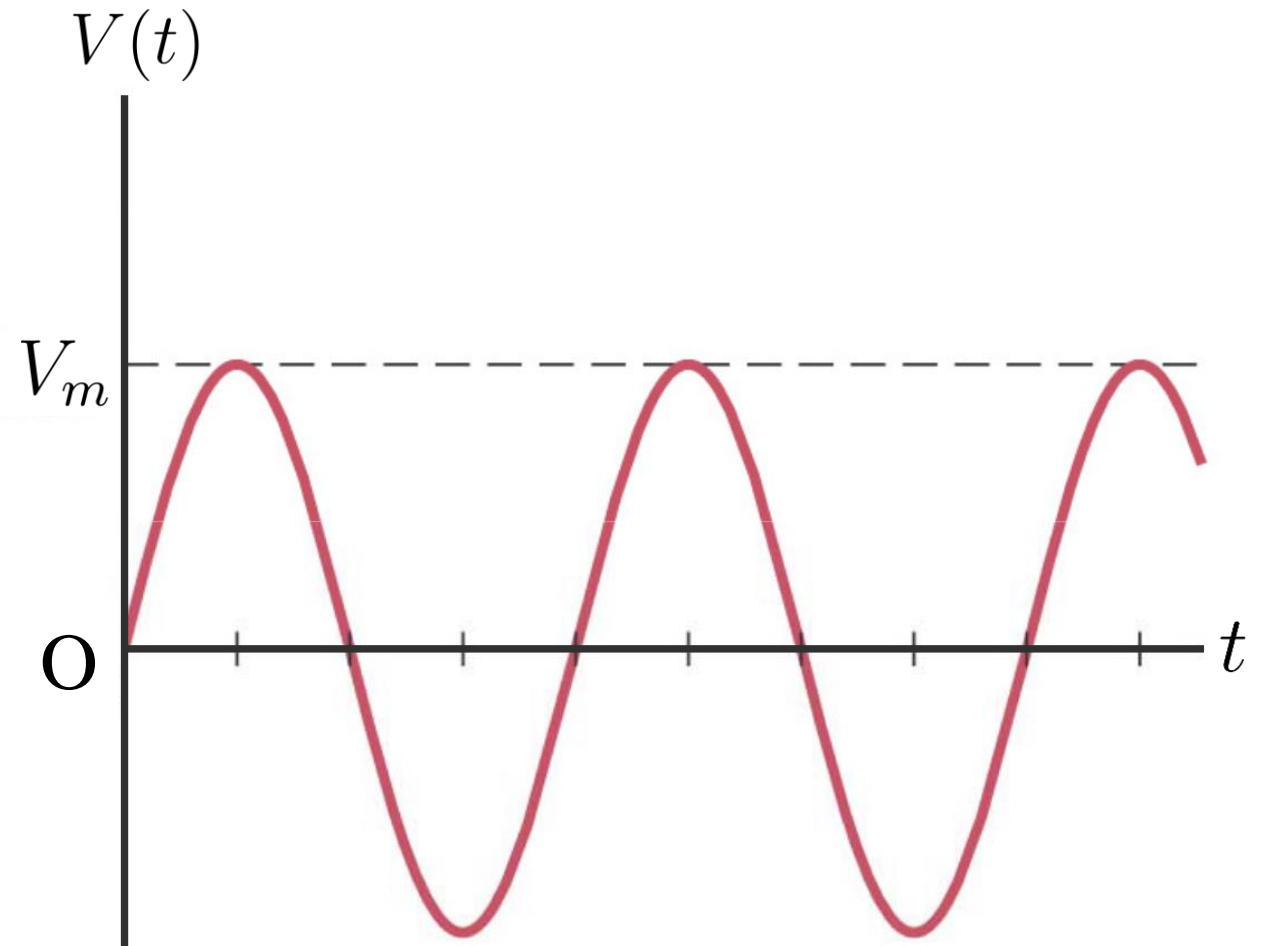

Average of $V(t)$ over time T

$$\bar{V} = \frac{1}{T} \int_0^T V(t) dt$$

$$V(t) = V_m \sin(\omega t)$$

$$\begin{aligned}\bar{V} &= \frac{V_m}{T} \int_0^T \sin(\omega t) dt \\ &= \frac{V_m}{T} \left[-\frac{\cos(\omega t)}{\omega} \right]_0^T \\ &= \frac{V_m}{\omega T} \{ -\cos(\omega T) + \cos 0 \} \\ &= \frac{V_m}{2\pi} \{ -\cos(2\pi) + \cos 0 \} \\ &= \frac{V_m}{2\pi} (-1 + 1) \\ &= 0.\end{aligned}$$



Average of $V(t)$ over time $T/2$

$$V_{\text{avg}} = \frac{1}{T/2} \int_0^{T/2} V(t) dt$$

$$V(t) = V_m \sin(\omega t)$$

$$\begin{aligned} V_{\text{avg}} &= \frac{2V_m}{T} \int_0^{T/2} \sin(\omega t) dt \\ &= \frac{2V_m}{T} \left[-\frac{\cos(\omega t)}{\omega} \right]_0^{T/2} \\ &= \frac{2V_m}{\omega T} \{ -\cos(\omega T/2) + \cos 0 \} \\ &= \frac{2V_m}{2\pi} \{ -\cos(\pi) + \cos 0 \} \\ &= \frac{2}{\pi} V_m \\ &\approx 0.637 V_m. \end{aligned}$$



The RMS value of $V(t)$

The term “RMS” stands for “Root-Mean-Squared”, also called the effective or heating value of alternating current, is equivalent to a DC voltage that would provide the same amount of heat generation in a resistor as the AC voltage would if applied to that same resistor.

RMS is not an “Average” voltage, and its mathematical relationship to peak voltage varies depending on the type of waveform.

$$V_{\text{rms}} = \left[\frac{1}{T} \int_0^T V^2(t) dt \right]^{1/2}$$



The RMS value of $V(t)$

$$\begin{aligned}V_{\text{rms}}^2 &= \frac{V_m^2}{T} \int_0^T \sin^2(\omega t) dt \\&= \frac{V_m^2}{2T} \int_0^T 2 \sin^2(\omega t) dt \\&= \frac{V_m^2}{2T} \int_0^T \{1 - \cos(2\omega t)\} dt \\&= \frac{V_m^2}{T} \int_0^T dt - \frac{V_m^2}{T} \int_0^T \cos(2\omega t) dt \\&= \frac{V_m^2}{2T} \left[T \right]_0^T - \frac{V_m^2}{2T} \left[\frac{\sin(2\omega t)}{2\omega} \right]_0^T\end{aligned}$$




The RMS value of $V(t)$

$$\begin{aligned}V_{\text{rms}}^2 &= \frac{V_m^2}{2} - \frac{V_m^2}{4\omega T} \left\{ \sin(2\omega T) - \sin(0) \right\} \\&= \frac{V_m^2}{2} - \frac{V_m^2}{4\omega T} \left\{ \sin(4\pi) - \sin(0) \right\} \\&= \frac{V_m^2}{2} - \frac{V_m^2}{4\omega T} (0 - 0) \\&= \frac{V_m^2}{2}.\end{aligned}$$

$$V_{\text{rms}} = \frac{V_m}{\sqrt{2}} \approx 0.707 V_m$$





The RMS and peak value of AC voltage

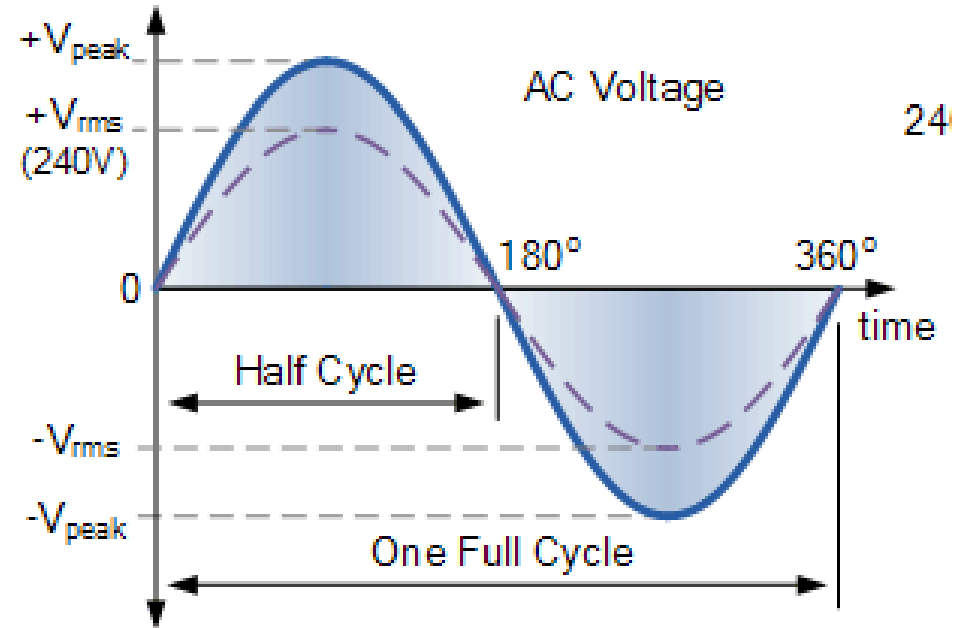


$$V_{\text{rms}} = \frac{V_m}{\sqrt{2}} \approx 0.707 V_m$$

Full-wave rectified signal

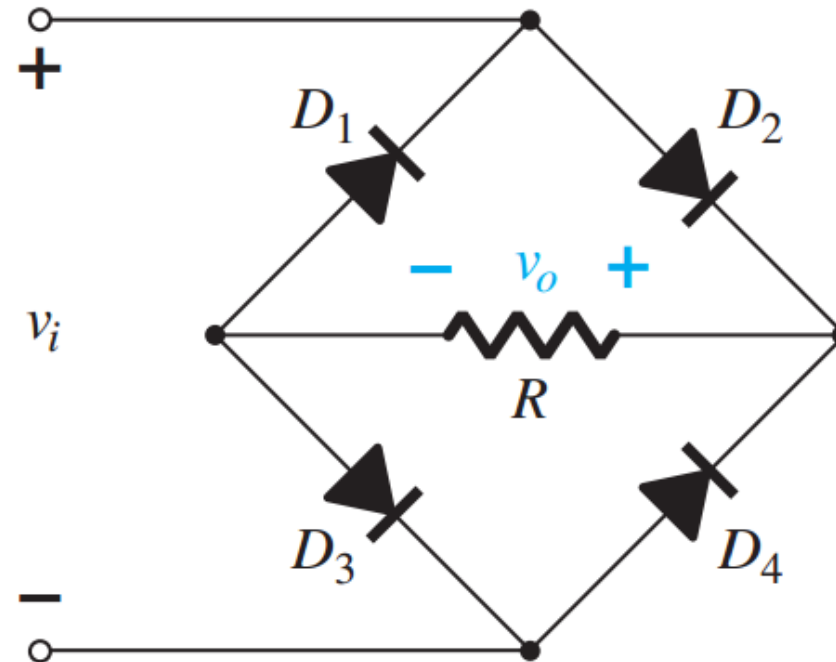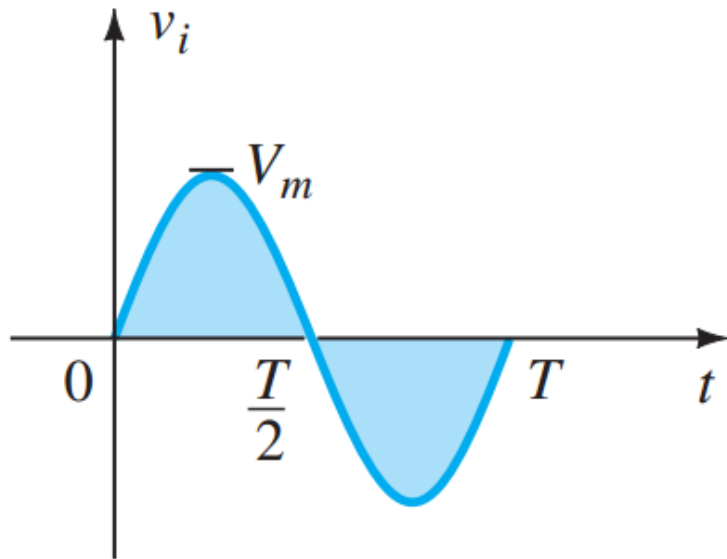

Electronic Devices and Circuit Theory – Boylestad, Nashelsky




Full-wave rectified signal

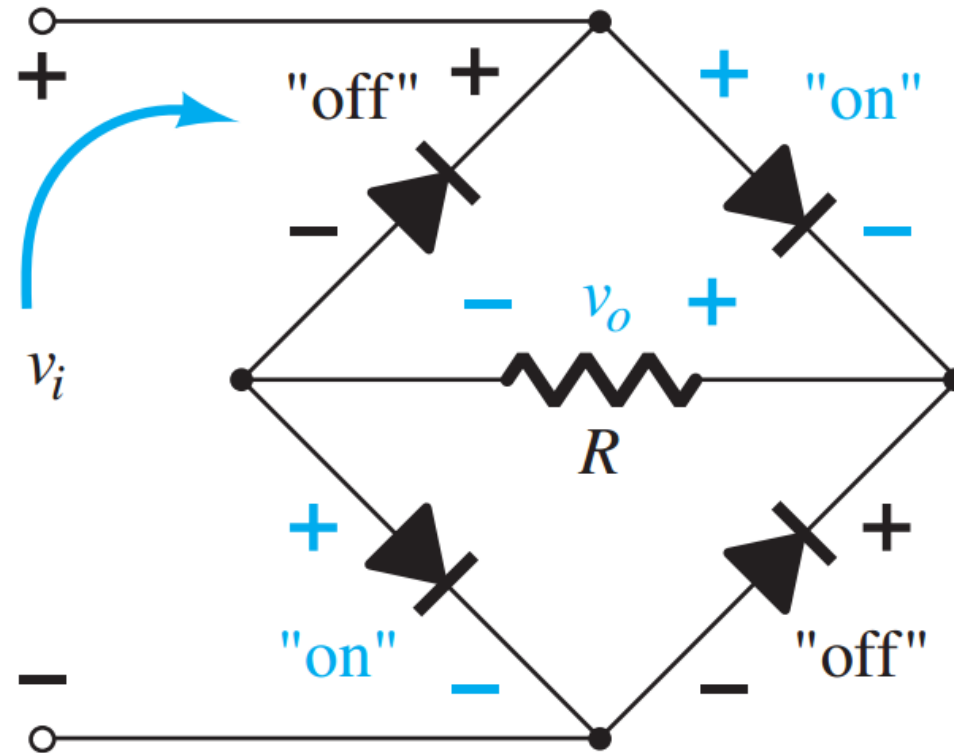

Electronic Devices and Circuit Theory – Boylestad, Nashelsky






Full-wave rectified signal

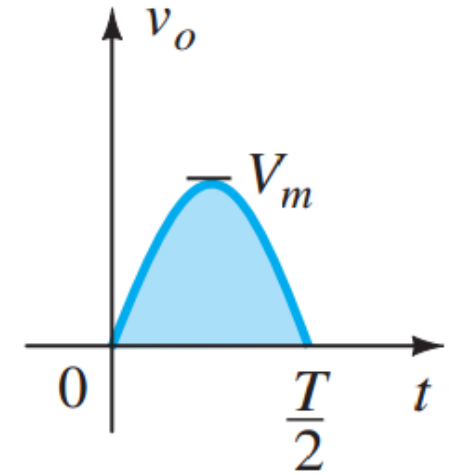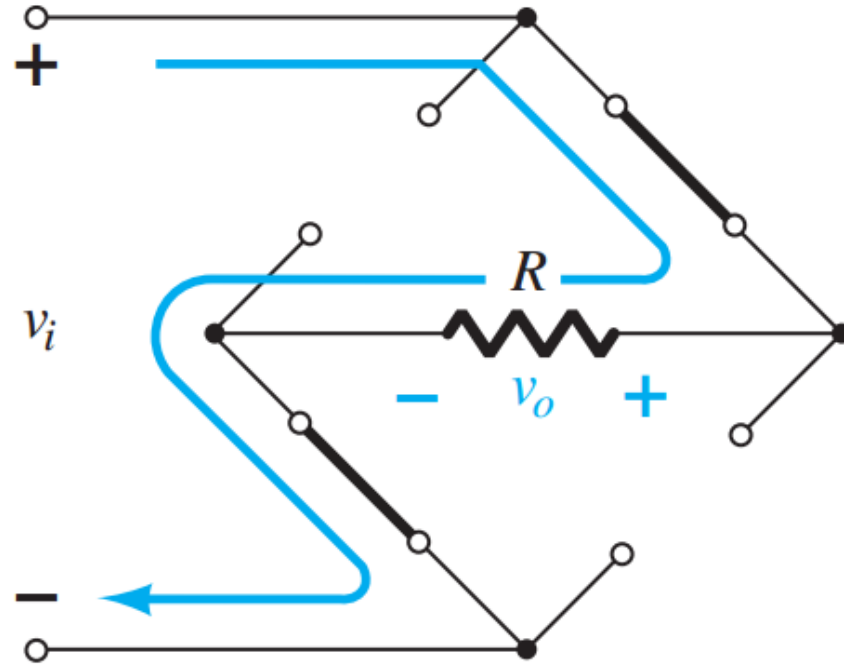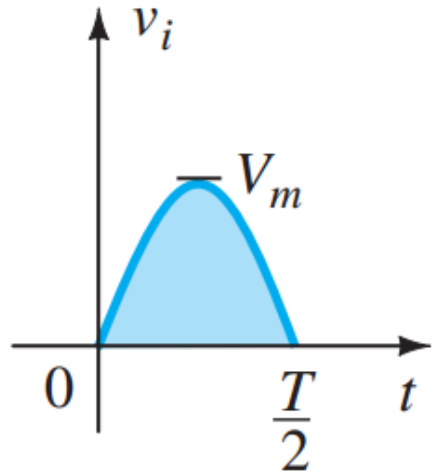

Electronic Devices and Circuit Theory – Boylestad, Nashelsky



Full-wave rectified signal

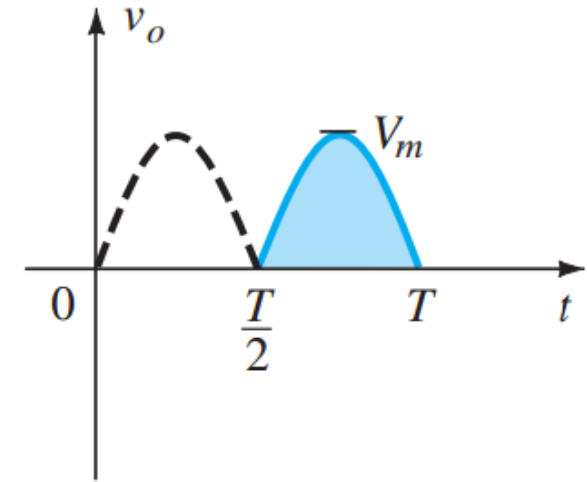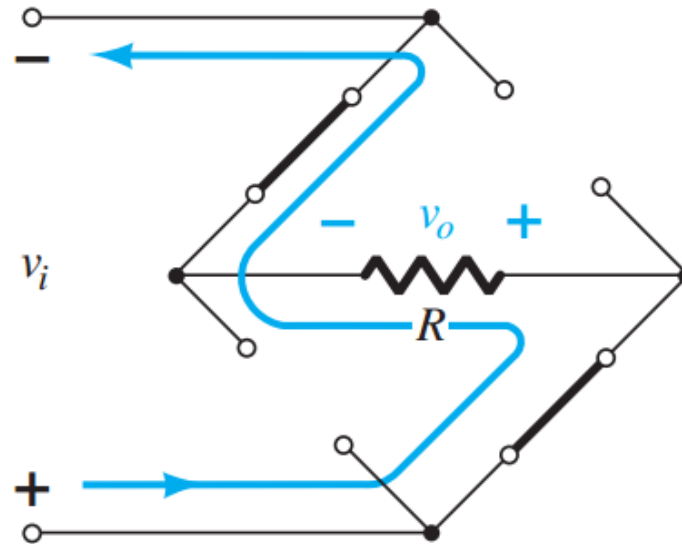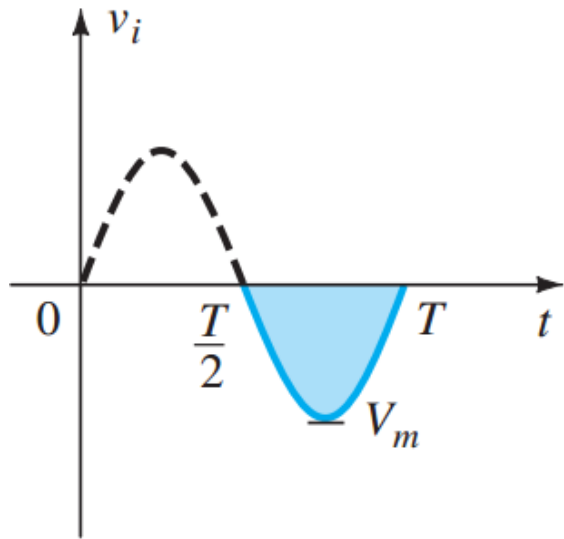

Electronic Devices and Circuit Theory – Boylestad, Nashelsky



Full-wave rectified signal

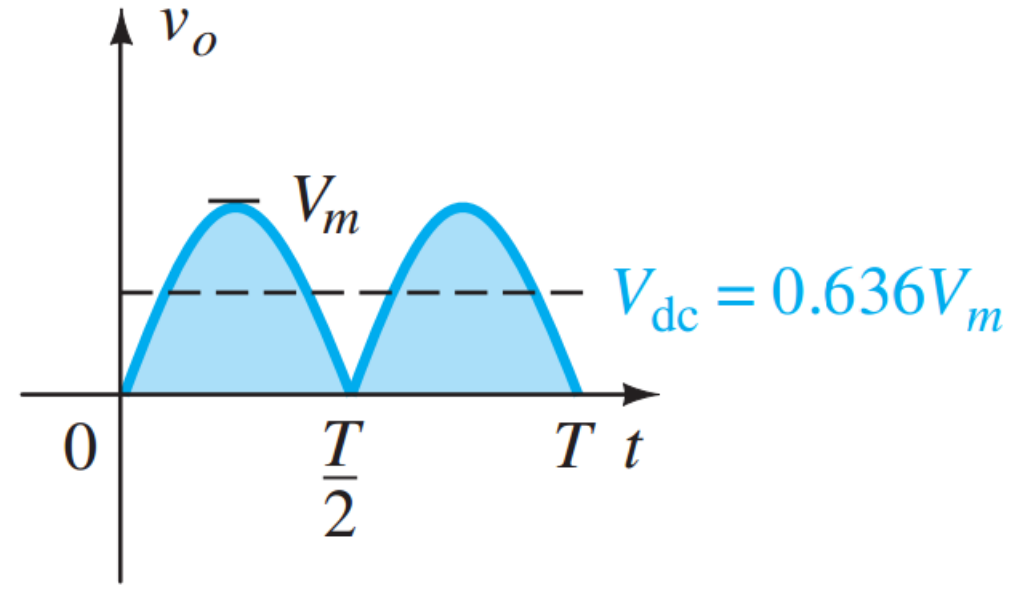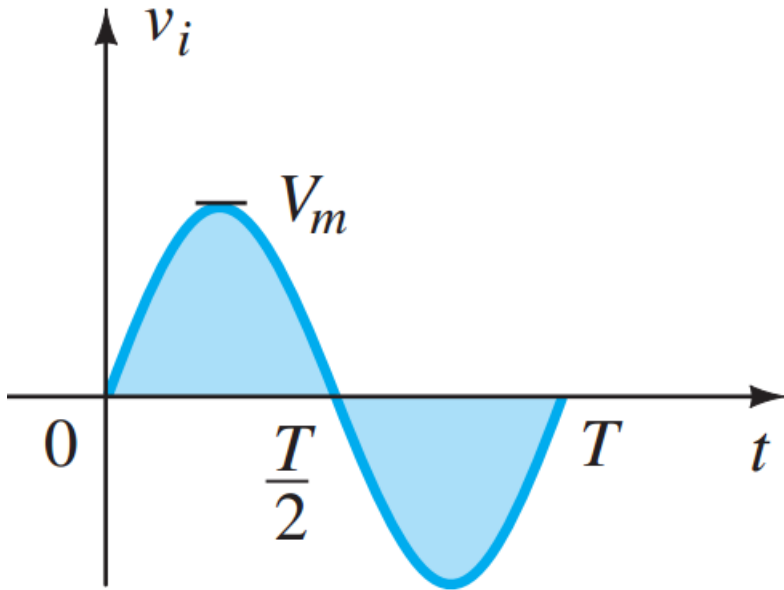



Electronic Devices and Circuit
Theory – Boylestad, Nashelsky

$$V_{dc} = 0.636 V_m$$

full-wave




Full-wave rectified signal

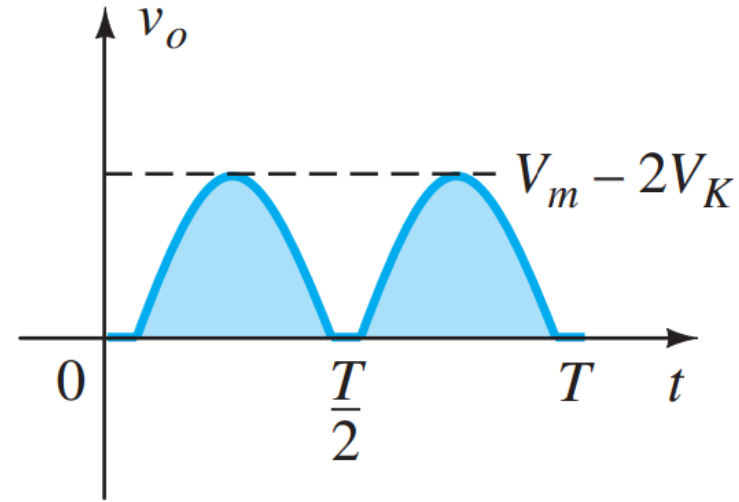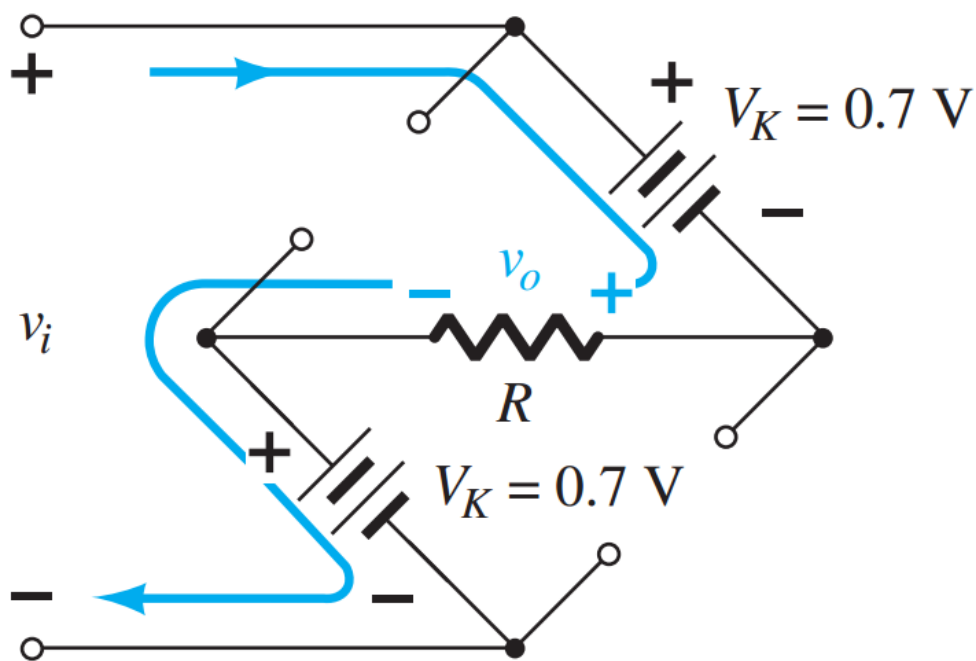


Electronic Devices and Circuit
Theory – Boylestad, Nashelsky

$$V_{dc} \cong 0.636(V_m - 2V_K)$$

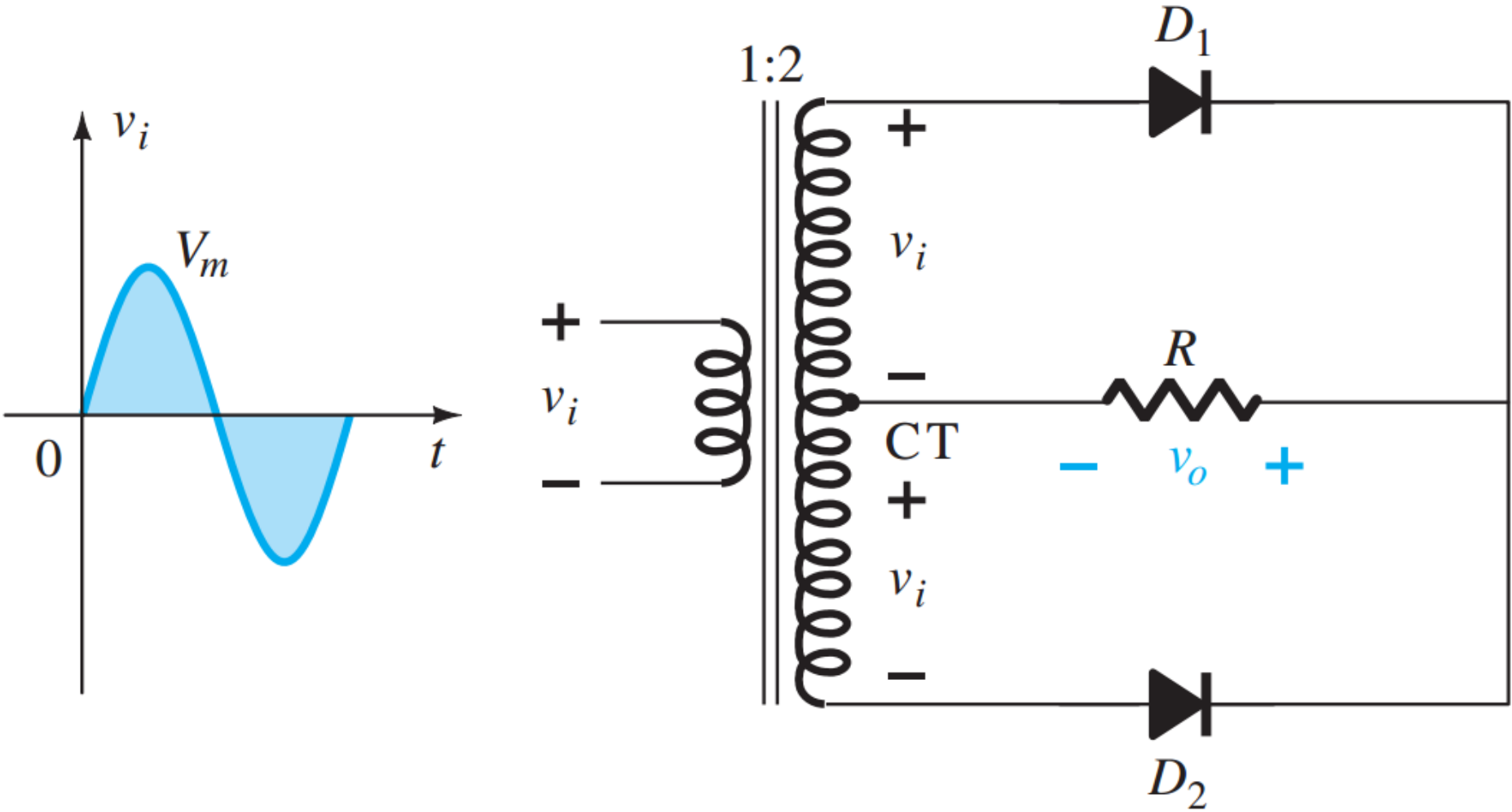Center-tapped transformer full-wave rectifier



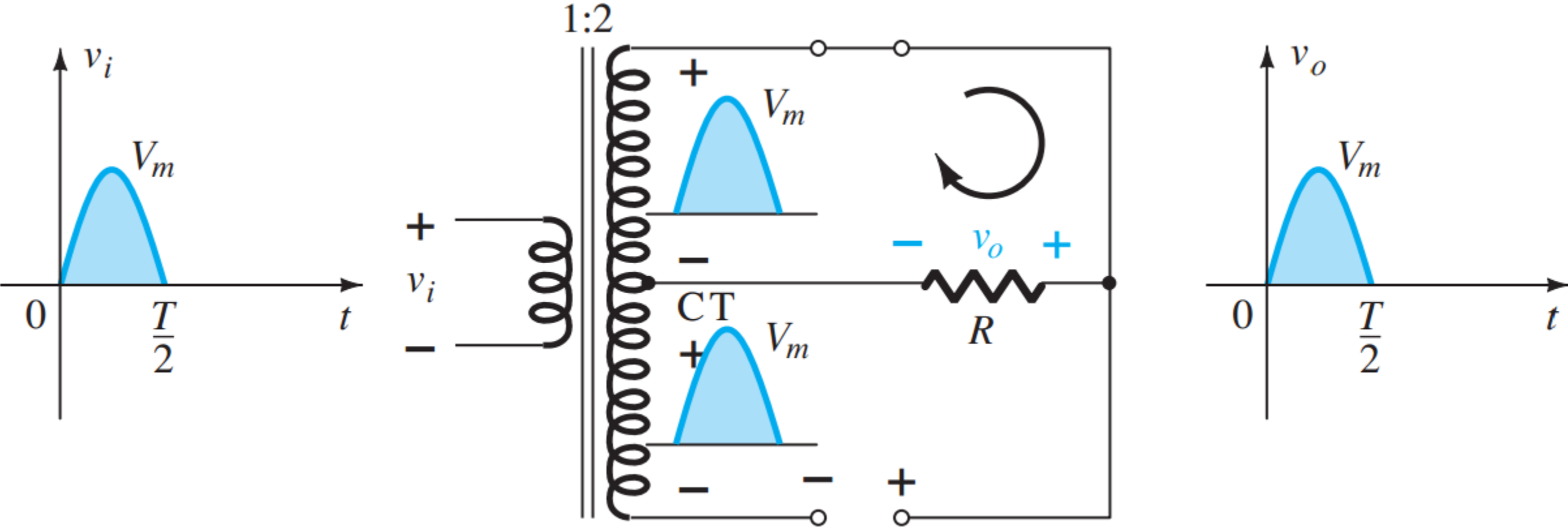Network conditions for the positive region of input voltage



Network conditions for the negative region of input voltage

